



Chapter 5


Sequential Logic

Sequential Circuits (1/2)

Combinational circuits:

- contain no memory elements
- the outputs depends on the current inputs

Sequential circuits:

 

- a feedback path
- outputs depends on present inputs and present states (pre. inputs)
- (inputs, current state) \Rightarrow (outputs, next state)
- synchronous: the transition happens at discrete instants of time
- asynchronous: at any instant of time

Sequential Circuits (2/2)

- A sequential circuit is specified by a time sequence of inputs, outputs and internal states

 


Fig. 5-1 Block Diagram of Sequential Circuit


Sequential circuits must be able to remember the past history

Flip-flops: most commonly used memory devices

A function of


- present inputs &
- present state of memory elements (the past sequence of inputs)

Clock

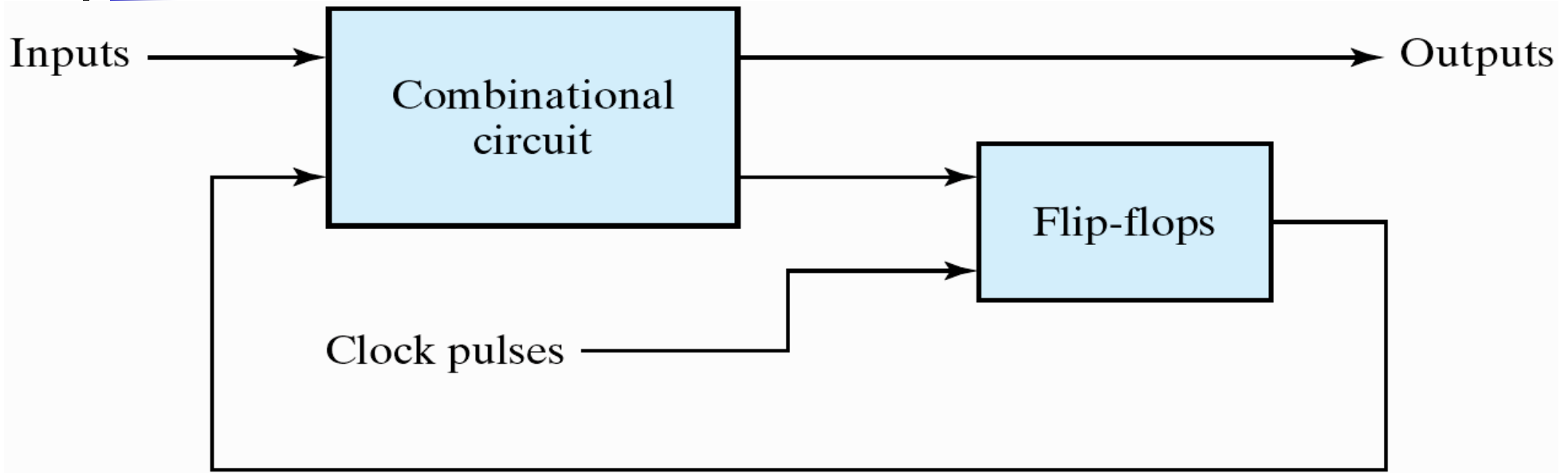

 (a) Block diagram

Use clock pulses generated by a clock generator



(b) Timing diagram of clock pulses

Fig. 5.2

Synchronous clocked sequential circuit




Types of Sequential Circuits


depending on the timing of their signals

- Synchronous (同步) sequential circuits
 - Storage elements are affected at discrete time instants
 - Use clock pulses in the inputs of storage elements
- Asynchronous (非同步) sequential circuits
 - Storage elements are affected at any time instant

Synchronous Sequential Circuits (1/2)

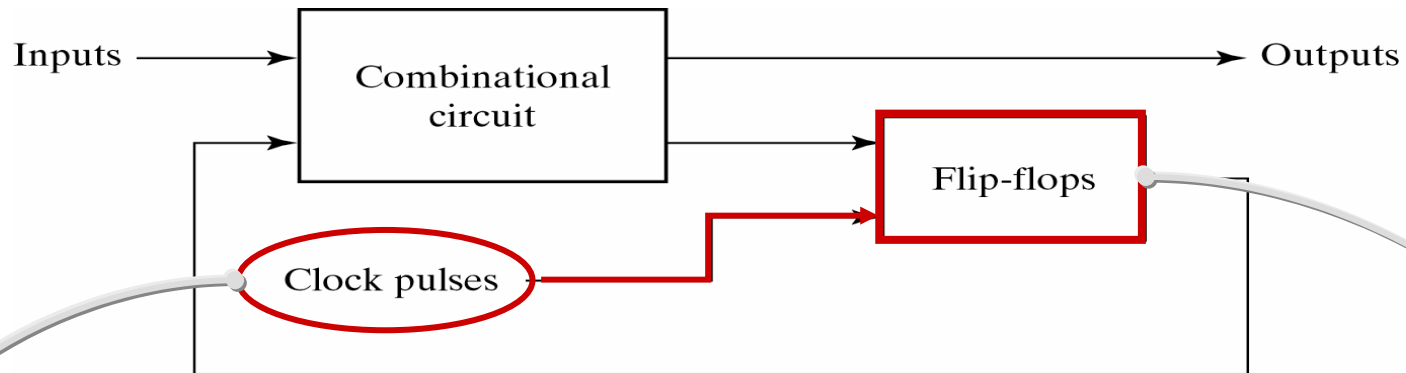

(a) Block diagram

 

(b) Timing diagram of clock pulses

Fig. 5-2 Synchronous Clocked Sequential Circuit

Synchronous

- Use clock pulses in the inputs of storage elements

Storage elements

- are affected only with the arrival of each pulse
- The storage elements used in the clocked sequential circuits are called "flip-flops"




Synchronous Sequential Circuits (2/2)

- Synchronous sequential circuits
 - a master-clock generator to generate a periodic train of clock pulses
 - the clock pulses are distributed throughout the system
 - clocked sequential circuits (most popular)
 - no instability problems
 - the memory elements: flip-flops
 - binary cells capable of storing one bit of information
 - two outputs: one for the normal value and one for the complement value
 - maintain a binary state indefinitely until directed by an input signal to switch states

Latches (1/3)

- The most basic types of flip-flops operate with signal levels → latch
- All FFs are constructed from the latches introduced here

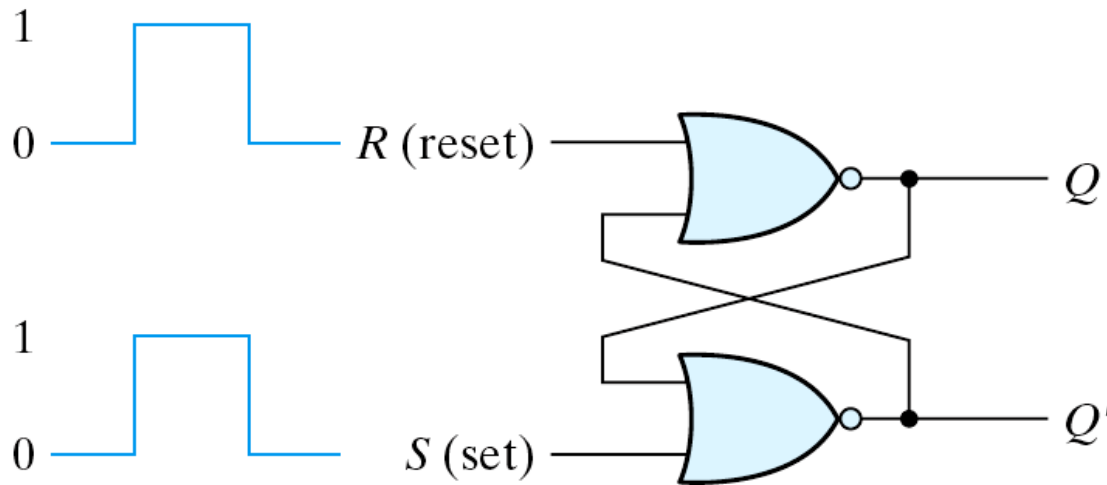A FF can maintain a binary state indefinitely until directed by an input signal to switch states





S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	(forbidden)

(b) Function table


Two NOR gates

Set → 1, Reset → 0


Latches (2/3)

  

 - Step 1: red number
- Step 2: yellow number
- Step 3: green number
- Step 4: black number




Latches (3/3)

 


S	R	P=Q'	Q	
0	0	*	*	// a stable state in the previous state
1	0	0	1	// change to another stable state "Set"
0	0	0	1	// remain in the previous state
0	1	1	0	// change to another stable state "Reset"
0	0	1	0	// remain in the previous state
1	1	0	0	// oscillate (unpredictable) if next SR=00

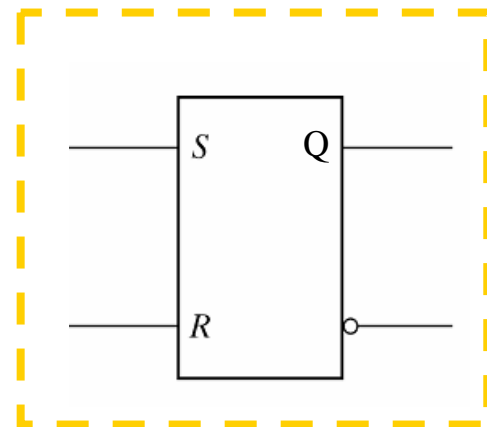- more complicated types can be built upon it the condition should be avoided
- an asynchronous sequential circuit
- (S,R) = (0,0): no operation
- (S,R) = (0,1): reset (Q=0, the clear state)
- (S,R) = (1,0): set (Q=1, the set state)
- (S,R) = (1,1): indeterminate state (Q=Q'=0)
- consider (S,R) = (1,1) ⇒ (0,0)



SR Latch with NAND gates

 


(a) Logic diagram

S	\overline{R}	Q	Q'	
$\overline{1}$	0	0	1	reset
1	1	0	1	set (after $S = 1, R = 0$)
0	1	1	0	
1	1	1	0	set (after $S = 0, R = 1$)
0	0	1	1	(forbidden)


(b) Function table

S'R' latch

 

(c) Graphic symbol

SR Latch with Control Input

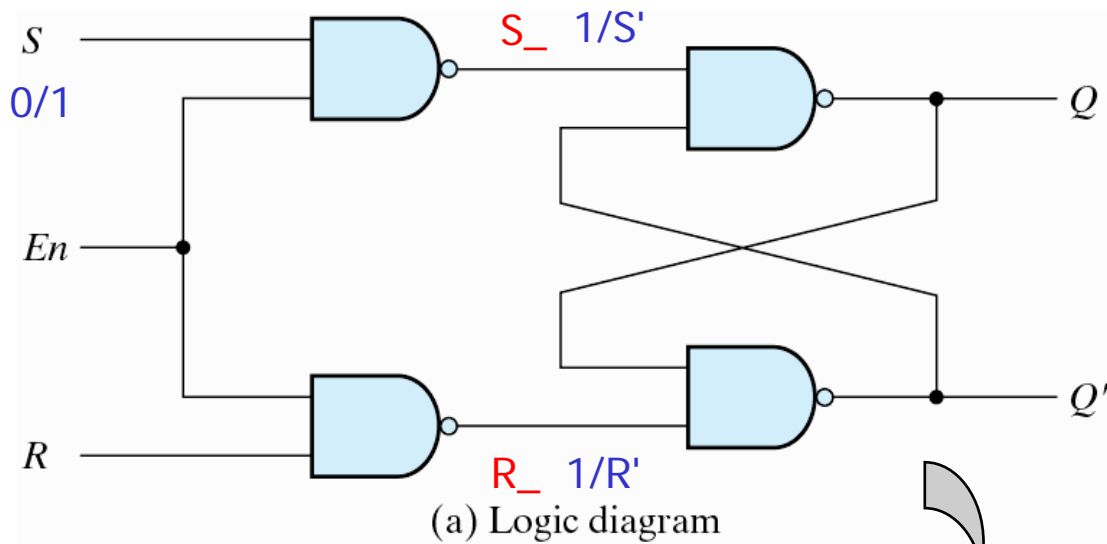


The complement output of the previous R'S' latch.

En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate


(b) Function table

$En=0$, no change
 $En=1$, enable

 


(c) Graphic symbol

$En=1$, no change
 $En=0$, enable

 

(c) Graphic symbol

D Latch (Transparent Latch)

 


(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

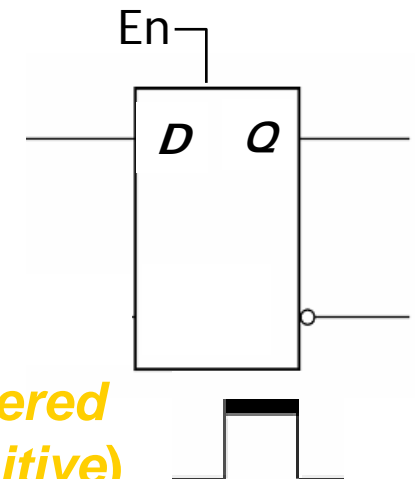(b) Function table


- eliminate the undesirable conditions of the indeterminate state in the RS flip-flop
- D: data
- gated D-latch
- $D \Rightarrow Q$ when $En=1$; no change when $En=0$




level triggered
(level-sensitive)

Flip-Flops

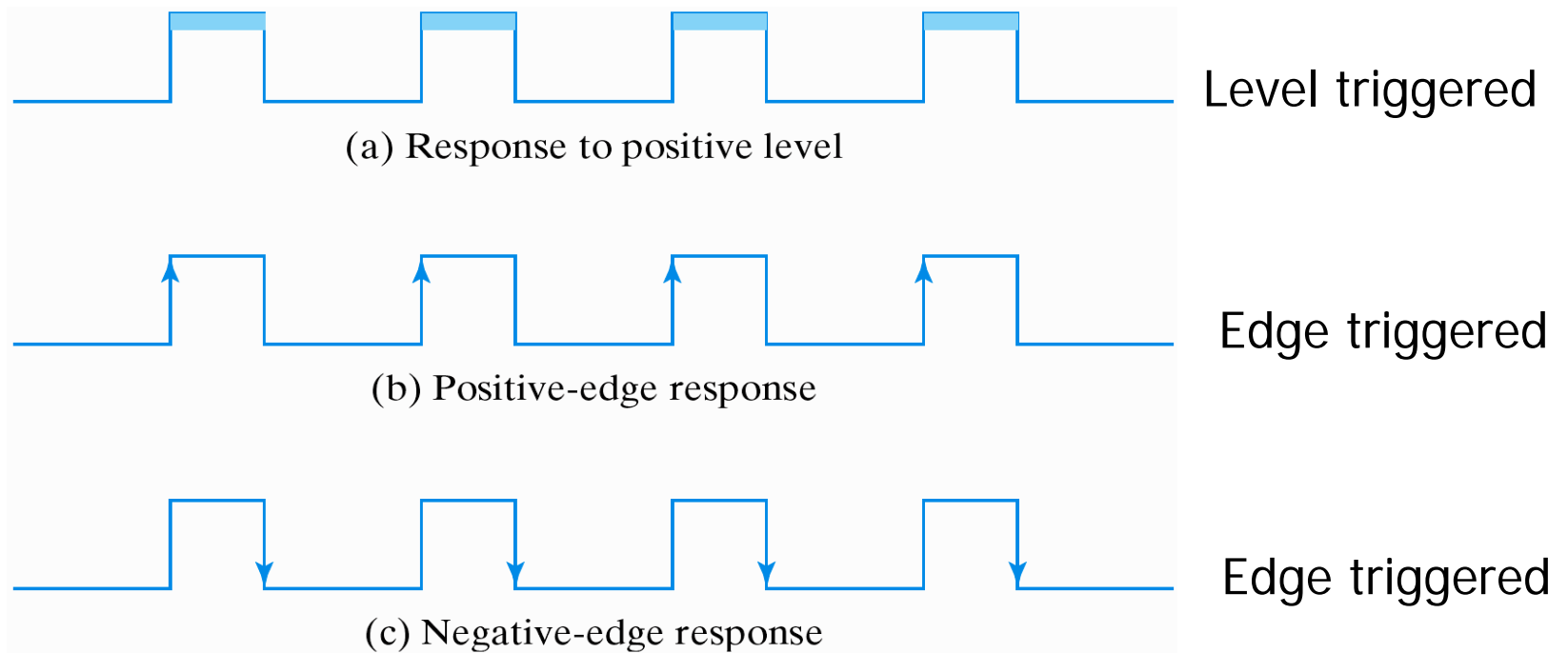- A trigger
 - The state of a latch or flip-flop is switched by a change of the control input
- Level triggered – latches
- Edge triggered – flip-flops



Problem of Latch

 

- If level-triggered flip-flops are used
 - the feedback path may cause instability problem (since the time interval of logic-1 is too long)
 - multiple transitions might happen during logic-1 level
- Edge-triggered flip-flops
 - the state transition happens only at the edge
 - eliminate the **multiple-transition** problem




Edge-Triggered D Flip-Flop

Two designs to solve the problem of latch:

- Master-slave D flip-flop
- Edge-trigger D flip-Flop



■ Master-slave D flip-flop

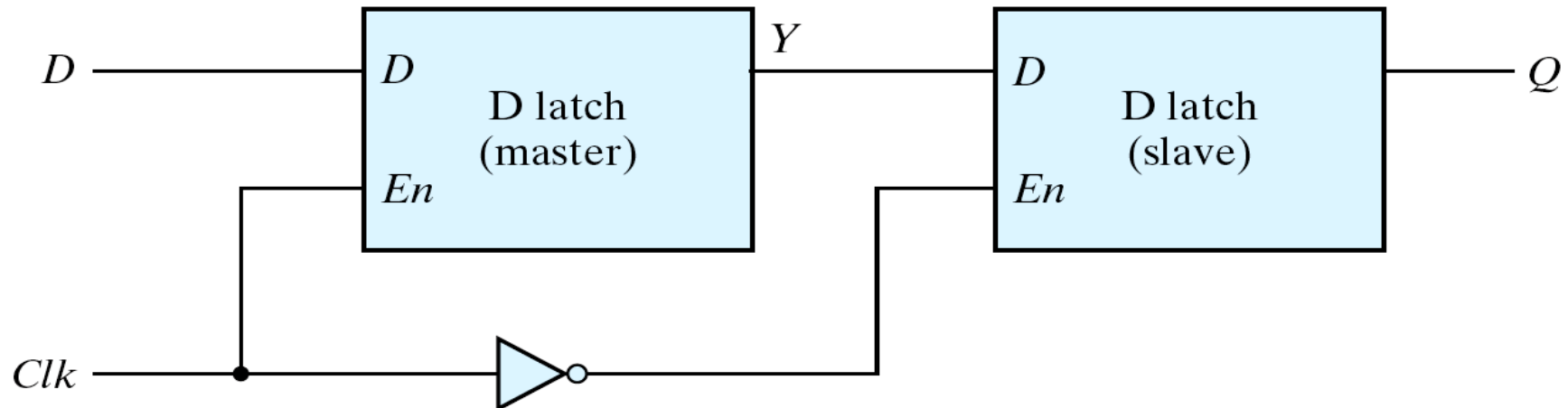- two separate flip-flops
- a master latch (positive-level triggered)
- a slave latch (negative-level triggered)





Master-slave D flip-flop (1/2)

 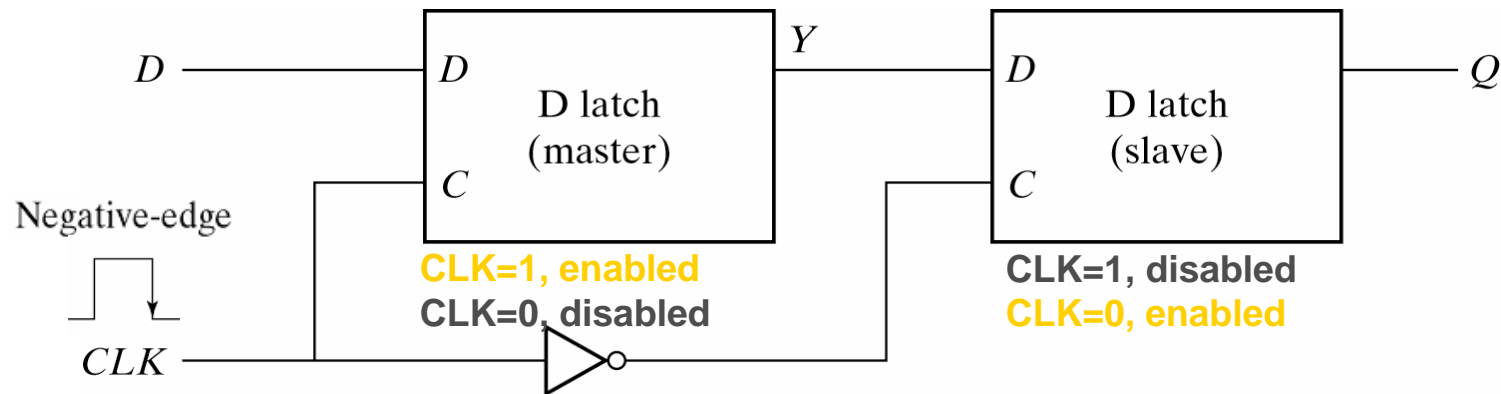- Two D latches and one inverter
- The circuit samples D input and changes its output Q only at the negative-edge of CLK
- isolate the output of FF from being affected while its input is changing



Master-slave D flip-flop (2/2)

  
- $CP = 1$: $(S,R) \Rightarrow (Y,Y')$; (Q,Q') holds
- $CP = 0$: (Y,Y') holds; $(Y,Y') \Rightarrow (Q,Q')$
- (S,R) could not affect (Q,Q') directly
- the state changes coincide with the negative-edge transition of CP



Edge-Triggered Flip-Flops (1/2)

the state changes during a clock-pulse transition

 A D-type positive-edge-triggered flip-flop



Three SR latches


Edge-Triggered Flip-Flops (2/2)

$(S,R) = (0,1): Q = 1$

$(S,R) = (1,0): Q = 0$

$(S,R) = (1,1):$ no operation

$(S,R) = (0,0):$ should be avoided

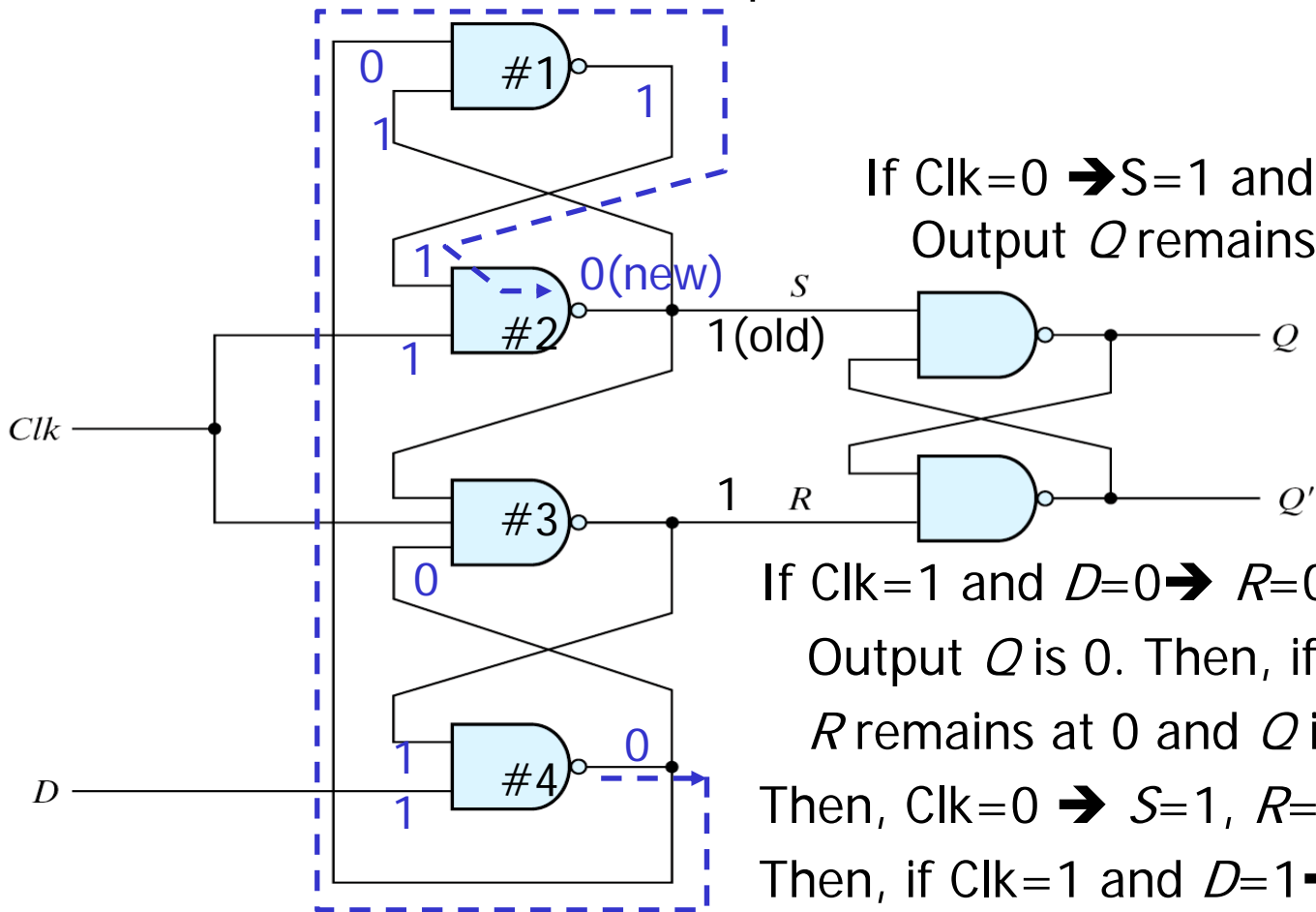

If $Clk=0 \rightarrow S=1$ and $R=1 \rightarrow$ no operation.
Output Q remains in the present state.

If $Clk=1$ and $D=0 \rightarrow R=0 \rightarrow$ Reset.

Output Q is 0. Then, if D changes to 1,
 R remains at 0 and Q is 0.

Then, $Clk=0 \rightarrow S=1, R=1 \rightarrow$ no operation ($Q=0$)

Then, if $Clk=1$ and $D=1 \rightarrow S=0 \rightarrow$ Set.

Output Q is 1. (see the blue dot-line flow)

Then, if D changes to 0, S remains at 0 and $Q=1$;




Positive-Edge-Triggered Flip-Flops

- Summary
 - $\text{Clk}=0$: $(S,R) = (1,1)$, no state change
 - $\text{Clk}=\uparrow$: state change once
 - $\text{Clk}=1$: state holds
 - eliminate the feedback problems in sequential circuits
- All flip-flops must make their transition at the same time

Flip-Flops

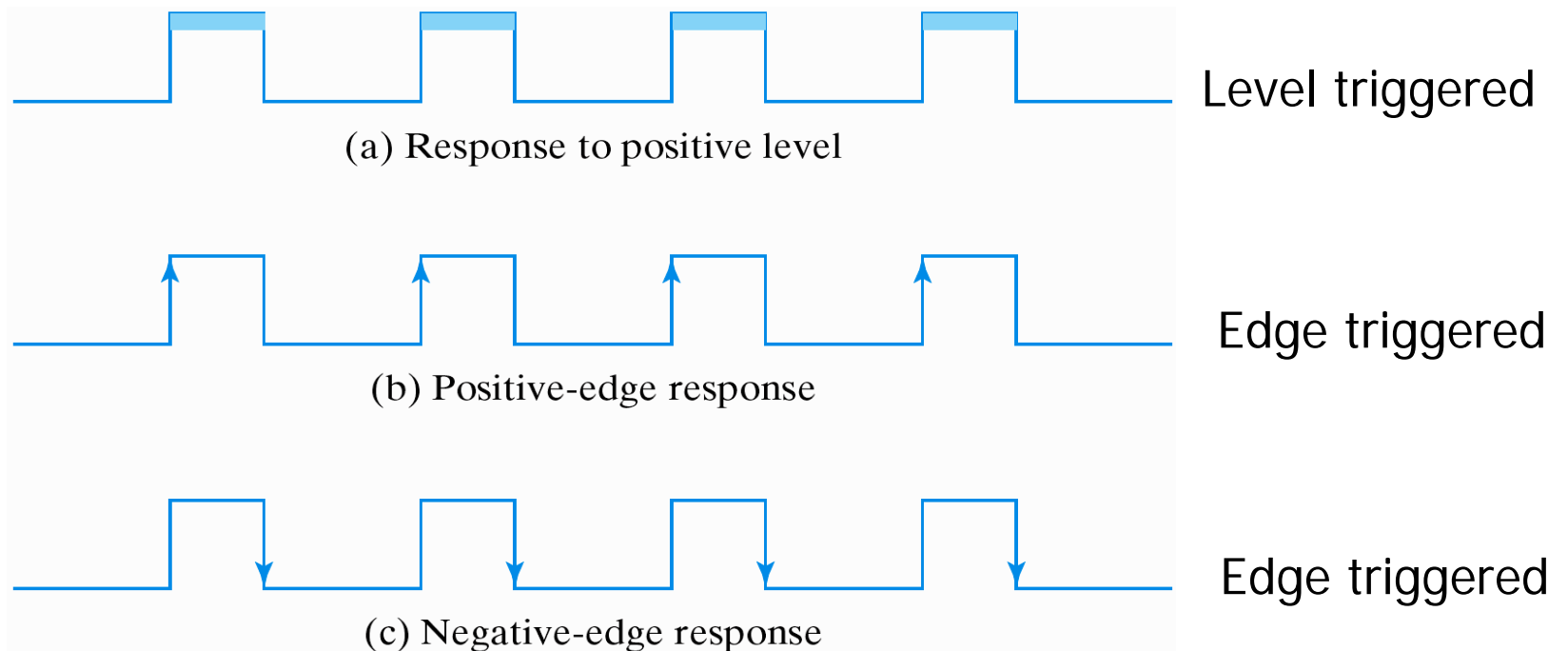- A trigger
 - The state of a latch or flip-flop is switched by a change of the control input
- Level triggered – latches
- Edge triggered – flip-flops






Setup Time and Hold Time


- The setup time
 - D input must be maintained at a constant value prior to the application of the positive Clk pulse
 - = the propagation delay through gates 4 and 1
 - data to the internal latches
- The hold time
 - D input must not changes after the application of the positive Clk pulse
 - = the propagation delay of gate 3 (try to understand)
 - clock to the internal latch

Timing Diagram

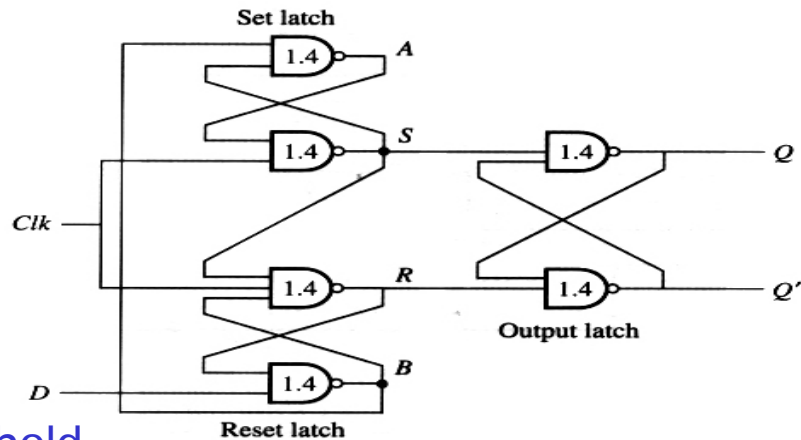

(a) Logic schematic


2.8 ns setup time
hold time 1.4 ns

 

 
(b) Timing diagram

Positive-Edge vs. Negative-Edge

- The edge-triggered D flip-flops
 - The most economical and efficient
 - The most popular flip-flop
 - Positive-edge and negative-edge




(a) Positive-edge

 



(a) Negative-edge

Latch vs. Flip-Flop

- Level triggered

 


Latch

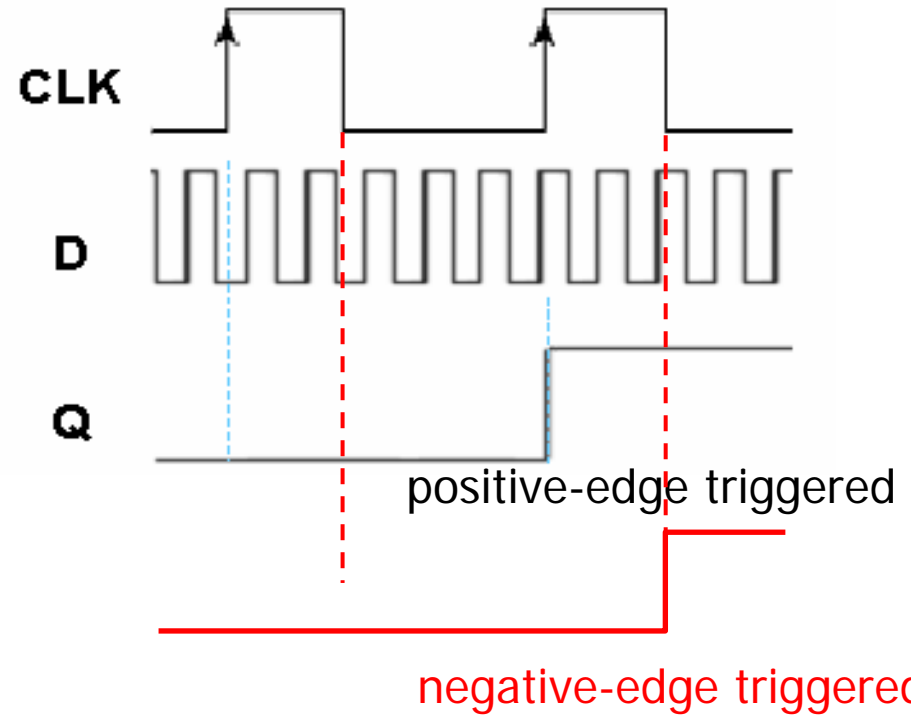 


positive-edge triggered

negative-edge triggered

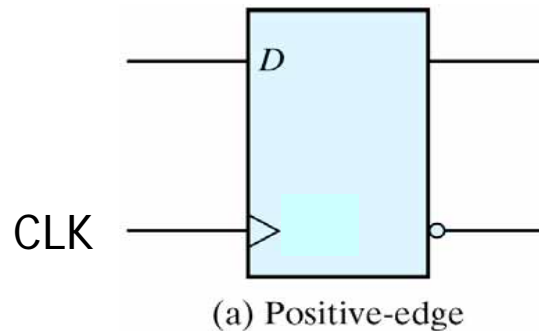


(a) Positive-edge

 


(a) Negative-edge

Clock Period

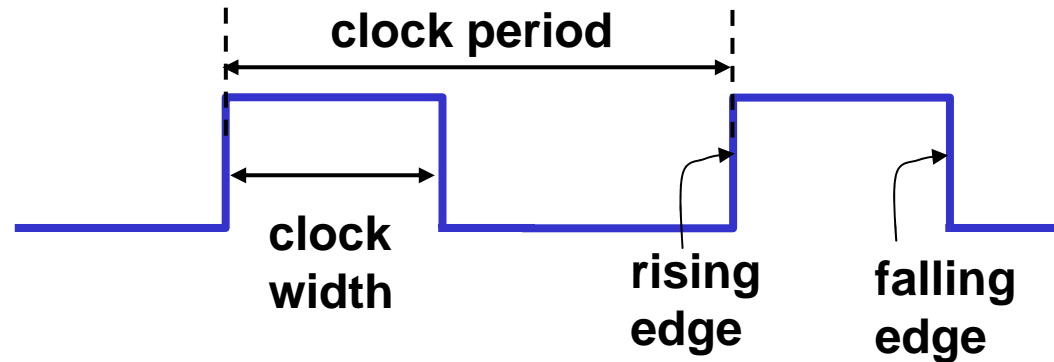

- Clock period (measured in micro or nanoseconds) is the time between successive transitions in the same direction
- Clock frequency (measured in MHz or GHz) is the reciprocal of clock period
- Clock width is the time interval during which clock is equal to 1
- Duty cycle is the ratio of the clock width and clock period
- Clock signal is active high if the changes occur at the rising edge or during the clock width. Otherwise, it is active low

Latch and Flip-Flop

 

Latches are level-sensitive since they respond to input changes during clock width. → Latches are difficult to work with for this reason.

Flip-Flops respond to input changes only during the change in clock signal (the rising edge or the falling edge).

They are easy to work with though more expensive than latches.

Two basic styles of flip-flops are available:


- (1) master-slave
- (2) edge-triggered

JK Flip-Flop

(*clear=1)


Inputs	J	K	D	Q(t+1)	Function
J, K disabled	0	0	Q(t)	Q(t)	no change
K enabled	0	1	0	0	reset FF to 0
J enabled	1	0	1	1	set FF to 1
J, K enabled	1	1	Q'(t)	Q'(t)	complement output

 All operations must be finished in the interval




	JK		J	
Q	00	01	11	10
0			1	1
1	1			1

$$D = JQ' + K'Q$$

 

positive-edge

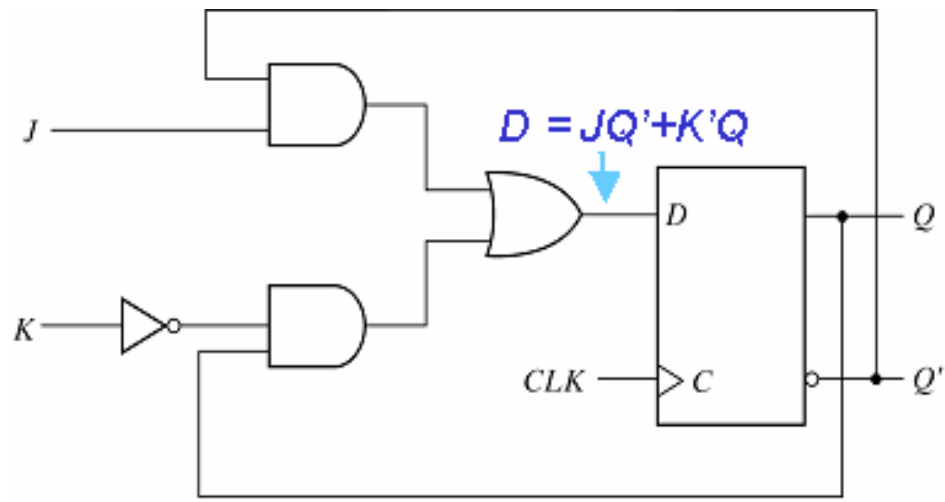

(a) Circuit diagram

(b) Graphic symbol

T(Toggle) Flip-Flop

Characteristic Table

T	Q(t+1)	
0	Q(t)	no change
1	Q'(t)	complement


“Complementing FF”

- $T=1$: a clock edge complements the output
- useful for designing binary counters

(a) based on JK FF

J	K	Q(t+1)	
0	0	Q(t)	no change
0	1	0	reset
1	0	1	set
1	1	Q'(t)	complement

- tie J,K together

 


(a) From JK flip-flop

(b) based on D FF


$$D = T \oplus Q = TQ' + T'Q$$

T	D	Q(t+1)	
0	Q	Q(t)	no change
1	Q'	Q'(t)	complement

Q	T	0	1
0			1
1	1		

 

(b) From D flip-flop

 

(c) Graphic symbol

Fig. 5-13 T Flip-Flop

Characteristic Equations/Tables of FFs

Characteristic Equations

- define next state $Q(t+1)$ as a function of inputs and present state algebraically

$$Q(t+1) = JQ' + K'Q$$

Characteristic Tables

- define next state $Q(t+1)$ as a function of inputs and present state $Q(t)$ in tabular form

Table 5.1
Flip-Flop Characteristic Tables

<i>JK Flip-Flop</i>			
<i>J</i>	<i>K</i>	<i>Q(t + 1)</i>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

D Flip-Flop

$$Q(t+1) = D$$

<i>D</i>	<i>Q(t + 1)</i>	
0	0	Reset
1	1	Set



T Flip-Flop

$$Q(t+1) = T \oplus Q = TQ' + T'Q$$

<i>T</i>	<i>Q(t + 1)</i>	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Direct inputs

 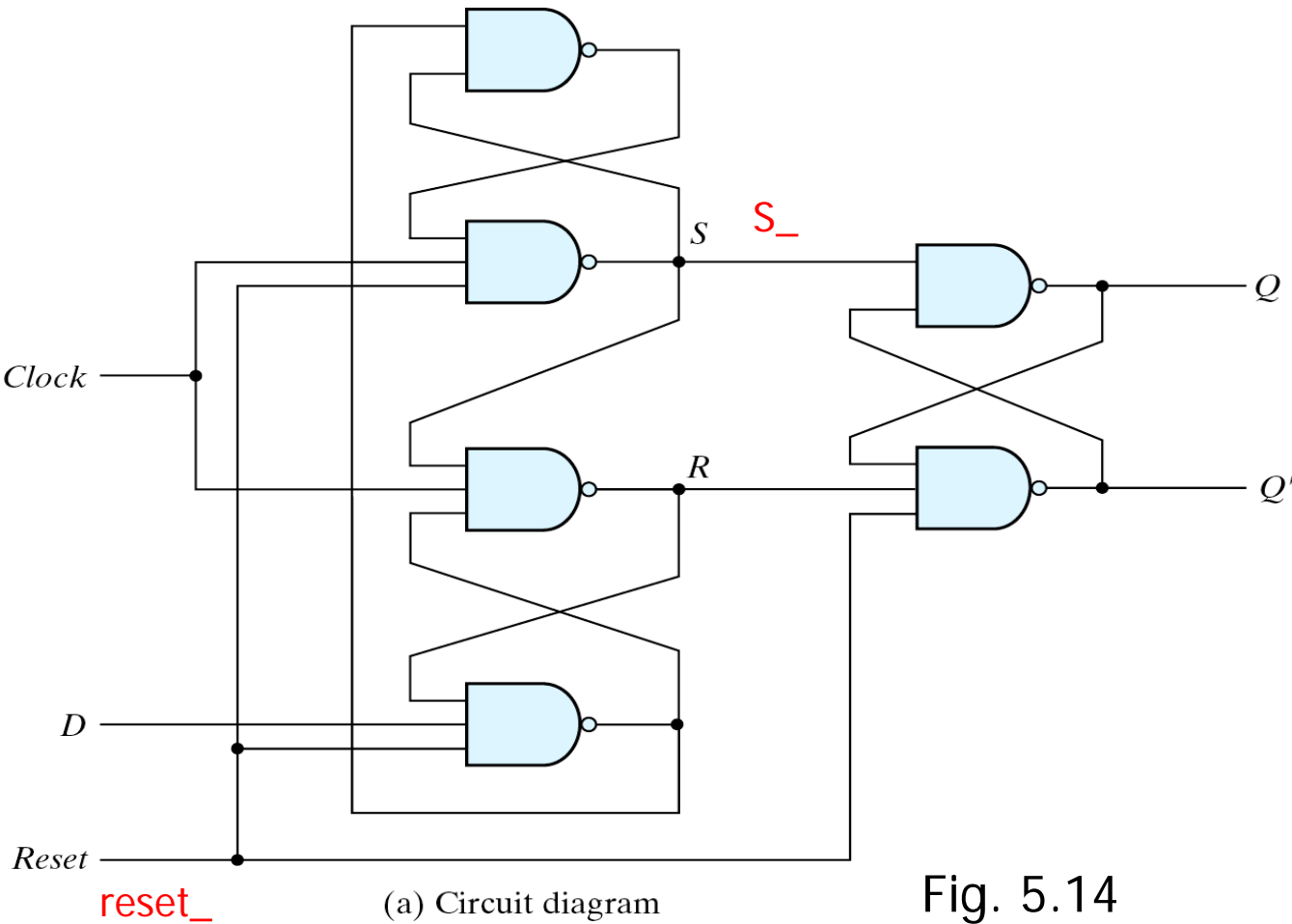- asynchronous set and/or asynchronous reset



(b) Graphic symbol

R	Clk	D	Q	Q'
0	X	X	0	1
0	↑	0	0	1
0	↑	1	1	0

(b) Function table


Fig. 5.14
D flip-flop with asynchronous reset




Direct Input

- Preset (PRE)
 - an asynchronous input that **sets** the FF
 - “direct set”
- Clear (CLR)
 - an asynchronous input that **clears** the FF
 - “direct reset”
- Purpose
 - Can be used to bring all FFs in a system to a known state prior to the clocked operation
- Asynchronous set: Set as soon as preset = 1
- Synchronous set: Set when preset=1 and CLK↑

D Flip-Flop with Asynchronous Reset

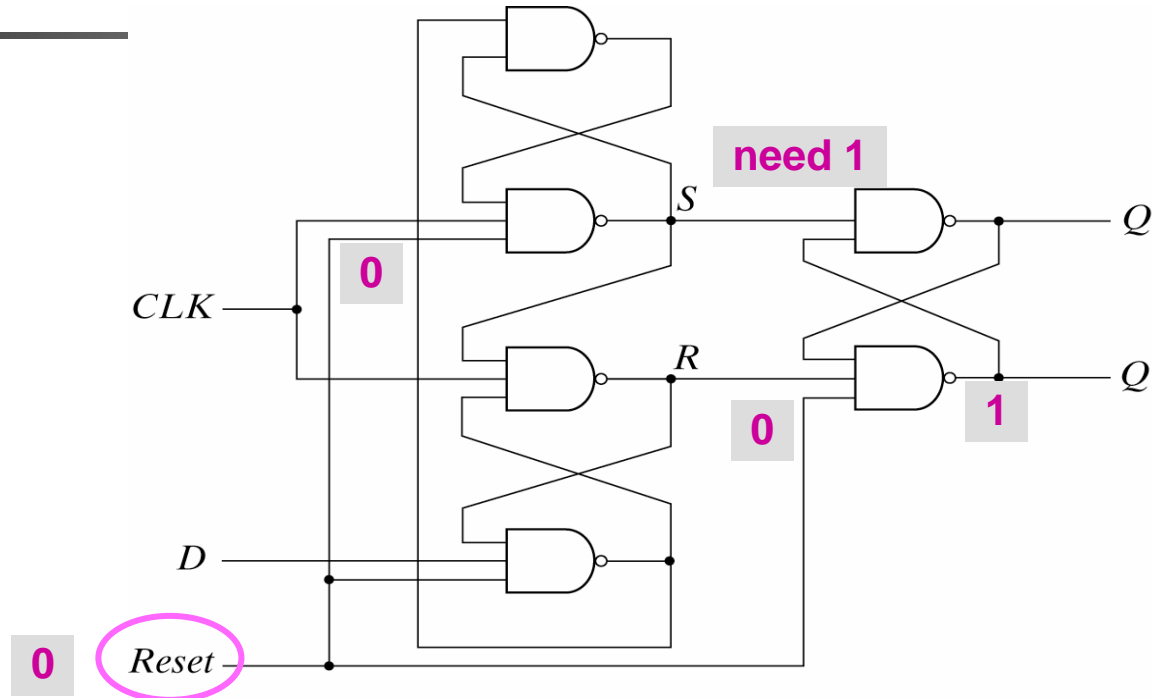

(a) Circuit diagram

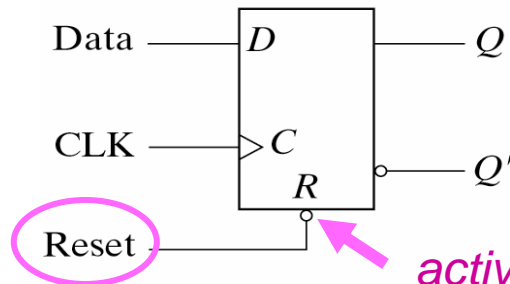

(b) Graphic symbol

reset →


<i>R</i>	<i>C</i>	<i>D</i>	<i>Q</i>	<i>Q'</i>
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

FF triggers on the positive edge of CLK

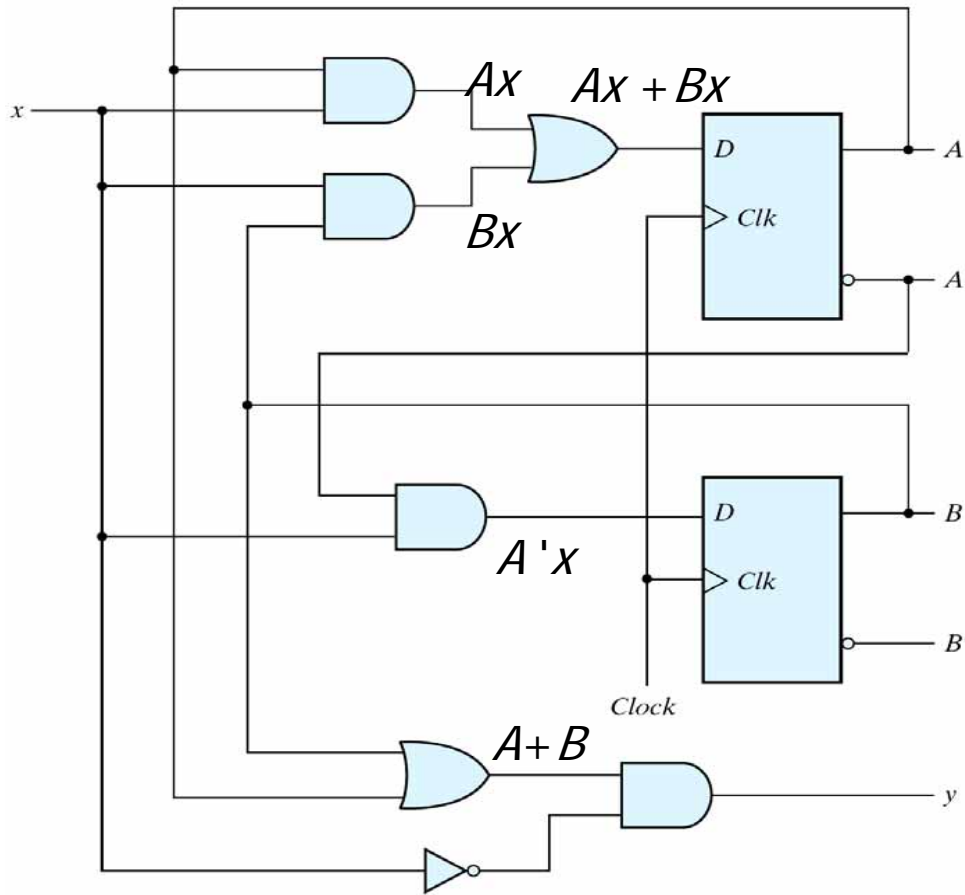(b) Function table

Analysis of Clocked Sequential Ckts

- A sequential circuit
 - (inputs, current state) \Rightarrow (output, next state)
 - a state transition table or state transition diagram



- State (transition) equation
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = A'(t)x(t)$
- A compact form
 - $A(t+1) = Ax + Bx$
 - $B(t+1) = A'x$
- The output equation
 - $y(t) = (A(t) + B(t))x'(t)$
 - $y = (A + B)x'$

State table 1

Table 5.2

State Table for the Circuit of Fig. 5.15

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

$$A(t+1) = Ax + Bx$$
$$B(t+1) = A'x$$
$$y = Ax' + Bx'$$

State table 2

$$A(t+1) = Ax + Bx$$

$$B(t+1) = A'x$$

$$y = Ax' + Bx'$$

Table 5.3

Second Form of the State Table

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>y</i>	<i>y</i>
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0


State diagram

- State transition diagram
 - a circle: a state
 - a directed lines connecting the circles: the transition between the states
 - Each directed line is labeled “inputs/outputs”

Table 5.3
Second Form of the State Table


Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

state: A B
input: x

 


Flip-Flop Input Equations

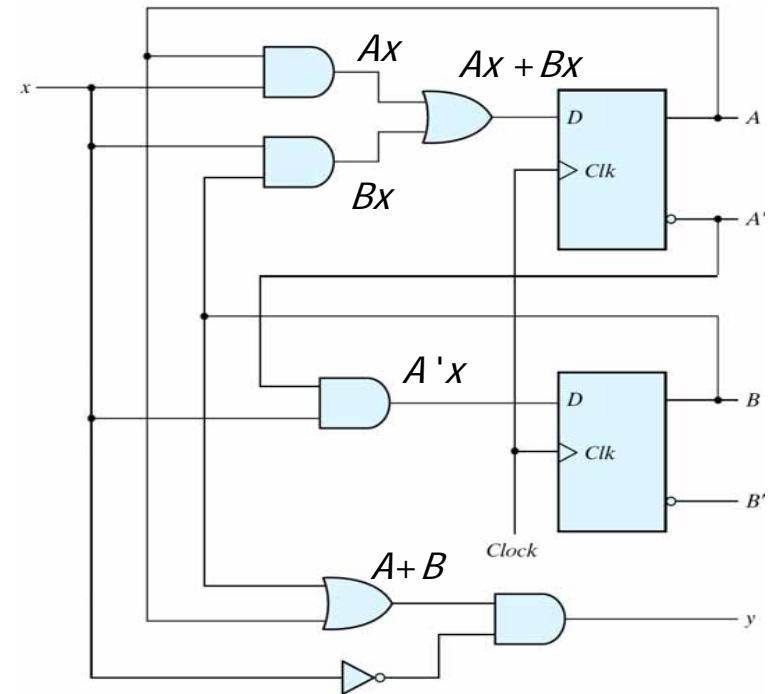- The part of circuit that generates the inputs to flip-flops
 - Also called excitation functions
 - $DA = Ax + Bx$
 - $DB = A'x$
- The output equations
 - to fully describe the sequential circuit
 - $y = (A+B)x'$



Analysis with D flip-flops

 
- The input equation
 - $D_A = A \oplus y$
- The state equation
 - $A(t+1) = A \oplus y$



(a) Circuit diagram

Present state	Inputs	Next state
<i>A</i>	<i>x y</i>	<i>A</i>
0	0 0	0
0	0 1	1
0	1 0	1
0	1 1	0
1	0 0	1
1	0 1	0
1	1 0	0
1	1 1	1

(b) State table

 

(c) State diagram

Analysis with JK flip-flops

- Determine the flip-flop input function in terms of the present state and input variables
- Used the corresponding flip-flop characteristic table to determine the next state

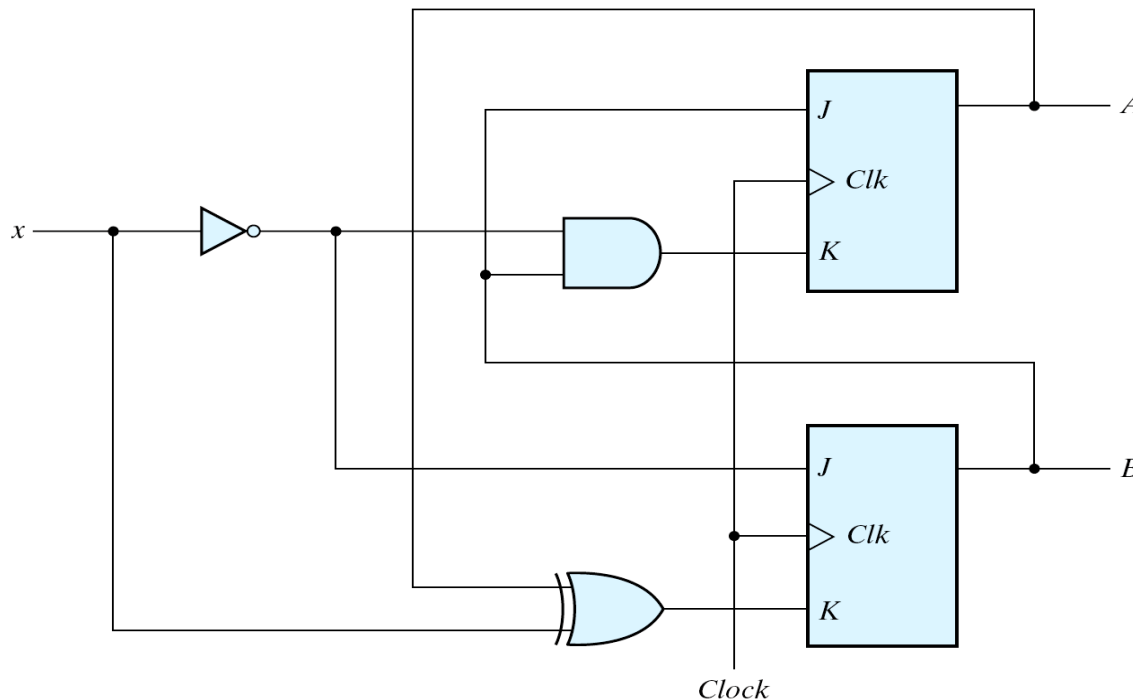


Fig. 5-18
Sequential circuit with
JK flip-flop

$$J_A = B, K_A = Bx'$$
$$J_B = x', K_B = A'x + A$$

State Table for Fig. 5-18

$$J_A = B, K_A = BX'$$

$$J_B = X', K_B = A'X + AX'$$

Table 5.4

State Table for Sequential Circuit with JK Flip-Flops

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

State Transition Diagram for Fig. 5-18

The characteristic equation of JK FF is

Method 1


$$A(t+1) = JA' + K'A_A$$

$$B(t+1) = JB' + K'B_B$$

State equation for A and B:

$$A(t+1) = BA' + (Bx')'A = A'B + AB' + Ax$$

$$B(t+1) = x'B + (A \oplus x)'B = B'x + ABx + A'Bx'$$

 

Method 2

	x	AB	00	01	11	10	
$A(t+1)$	0		0	1	0	1	AB'
	1		0	1	1	1	$A'B$ Ax

Using K-map, we also can derive $A(t+1)$.

$$A(t+1) = A'B + AB' + Ax$$


Table 5.4

State Table for Sequential Circuit with JK Flip-Flops

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

Analysis with T Flip-Flops

 - The characteristic equation
 - $Q(t+1) = T \oplus Q = TQ' + T'Q$




(a) Circuit diagram

Table 5.5

State Table for Sequential Circuit with T Flip-Flops

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

 


(b) State diagram


Finite State Machine (FSM)

The inputs, outputs and states of a sequential circuit can be described as the FSM. There are two different FSMs:

 (a) Mealy machine: the outputs are functions of both the present state and inputs




 (b) Moore machine: the outputs are functions of the present state only




Mealy Machine vs. Moore Machine

Mealy Machine

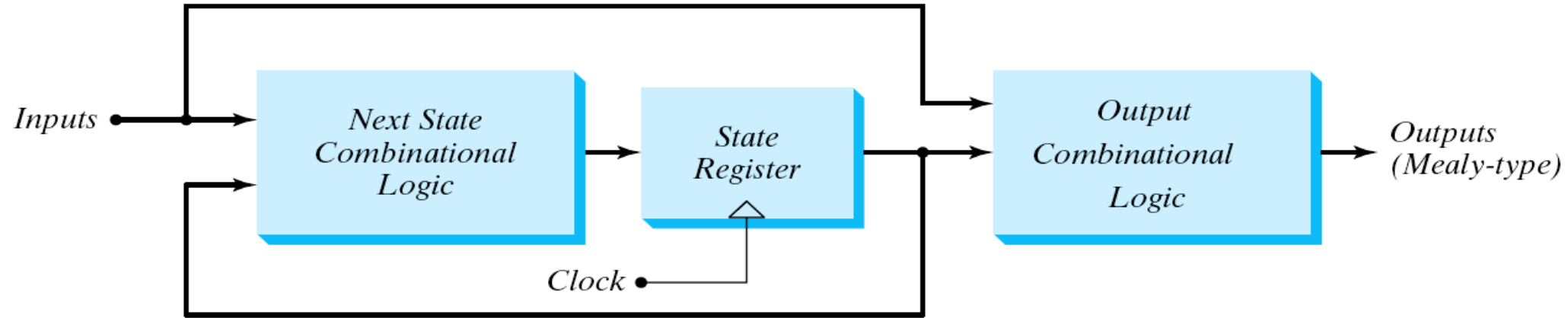

(a)

Moore Machine

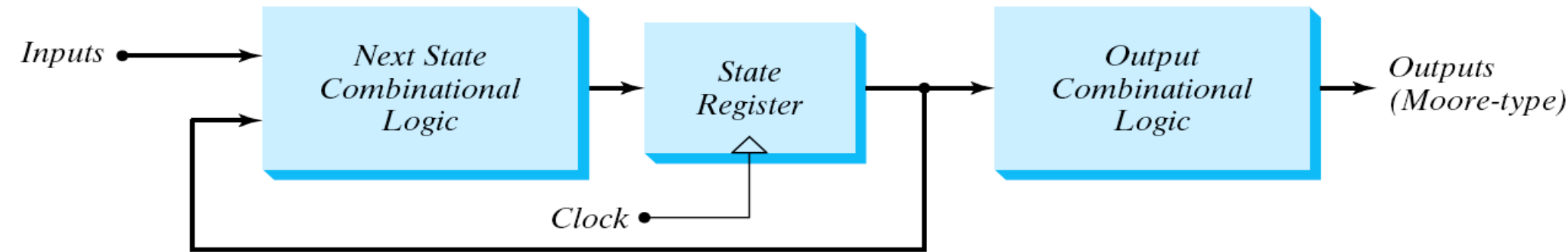


(b)

State Reduction and Assignment

State Reduction

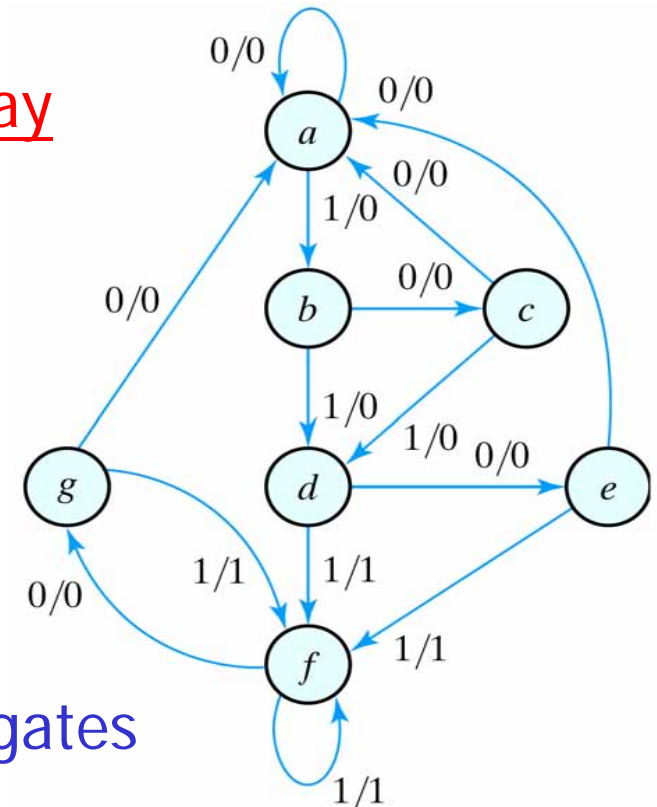- reductions on the number of flip-flops and the number of gates
- a reduction in the number of states may result in a reduction in the number of flip-flops
- How to reduce the necessary states?



State reduction:

does not guarantee a saving in #FFs or #gates

State Reduction

■ state a a b c d e f f g f g a
input 0 1 0 1 0 1 1 0 1 0 0
output 0 0 0 0 0 1 1 0 1 0 0

- only the input-output sequences are important
- two circuits are equivalent
 - have identical outputs for all input sequences
 - the number of states is not important

 


Fig. 5.25 State diagram

Equivalent States

- Two states are said to be equivalent
 - for each member of the set of inputs, they give exactly the same output and send the circuit to the same state or to an equivalent state
 - one of them can be removed

 


Table 5.6
State Table

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Reducing State Table

Table 5.7
Reducing the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1

Reduced Finite State Machine

Table 5.8
Reduced State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1


■ state a a b c d e d d e d e a
 input 0 1 0 1 0 1 1 0 1 0 0
 output 0 0 0 0 0 1 1 0 1 0 0

State Reduction

- the checking of each pair of states for possible equivalence can be done systematically (9-5)
- the unused states are treated as don't-care condition \Rightarrow fewer combinational gates

This example:

 7 states $\xrightarrow{\text{reduce to}}$ 5 states





State Assignment

- to minimize the cost of the combinational circuits (not easy certainly ??)
- three possible binary state assignments

Table 5.9

Three Possible Binary State Assignments

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000



Binary Assignment

- any binary number assignment is satisfactory as long as each state is assigned a unique number

both OK → 000,001,010,011,100 (OK v)

→ 011,100,101,110,111 (OK v)

Table 5.10

Reduced State Table with Binary Assignment 1

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1

The Three Assignments

- Binary code
 - n-bit code for m states, $2^n \geq m$ (n FFs)
- Gray code
 - n-bit code for m states, $2^n \geq m$ (n FFs)
 - More suitable for K-map simplification
(more possible lower power)
- One-hot
 - m-bit code for m states (m FFs)
 - often used in control design

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000



Design Procedure

- specification → a state diagram (most challenging)
- state reduction if necessary
- assign binary values to the states
- obtain the binary-coded state table
- choose the type of flip-flops
- derive the simplified flip-flop input equations and output equations
- draw the logic diagram

Synthesis

The part of design that follows a well-defined procedure is called synthesis. Once a spec has been set down and the state diagram obtained, it is possible to use known synthesis procedure to complete the design.

Synthesis using D flip-flops (1/2)

- An example state diagram and state table

Design a circuit that detects one to three or more consecutive 1's in a input string

 


Table 5.11
State Table for Sequence Detector

Present State		Input		Next State		Output
A	B	x		A	B	y
0	0	0	m_0	0	0	0
0	0	1	m_1	0	1	0
0	1	0	m_2	0	0	0
0	1	1	m_3	1	0	0
1	0	0	m_4	0	0	0
1	0	1	m_5	1	1	0
1	1	0	m_6	0	0	1
1	1	1	m_7	1	1	1

Synthesis using D flip-flops (2/2)

- The flip-flop input equations


$$(1) A(t+1) = D_A(A,B,x) = (3,5,7)$$

$$(2) B(t+1) = D_B(A,B,x) = (1,5,7)$$

- The output equation

$$(3) y(A,B,x) = (6,7)$$

 - Logic minimization using **three** K maps



Logic Diagram of Sequence Detector with D FF

- FF Input eqs.

$$D_A(A,B,x) = Ax+Bx$$

$$D_B(A,B,x) = Ax+B'x$$

- Output eq.

$$y(A,B,x) = AB$$

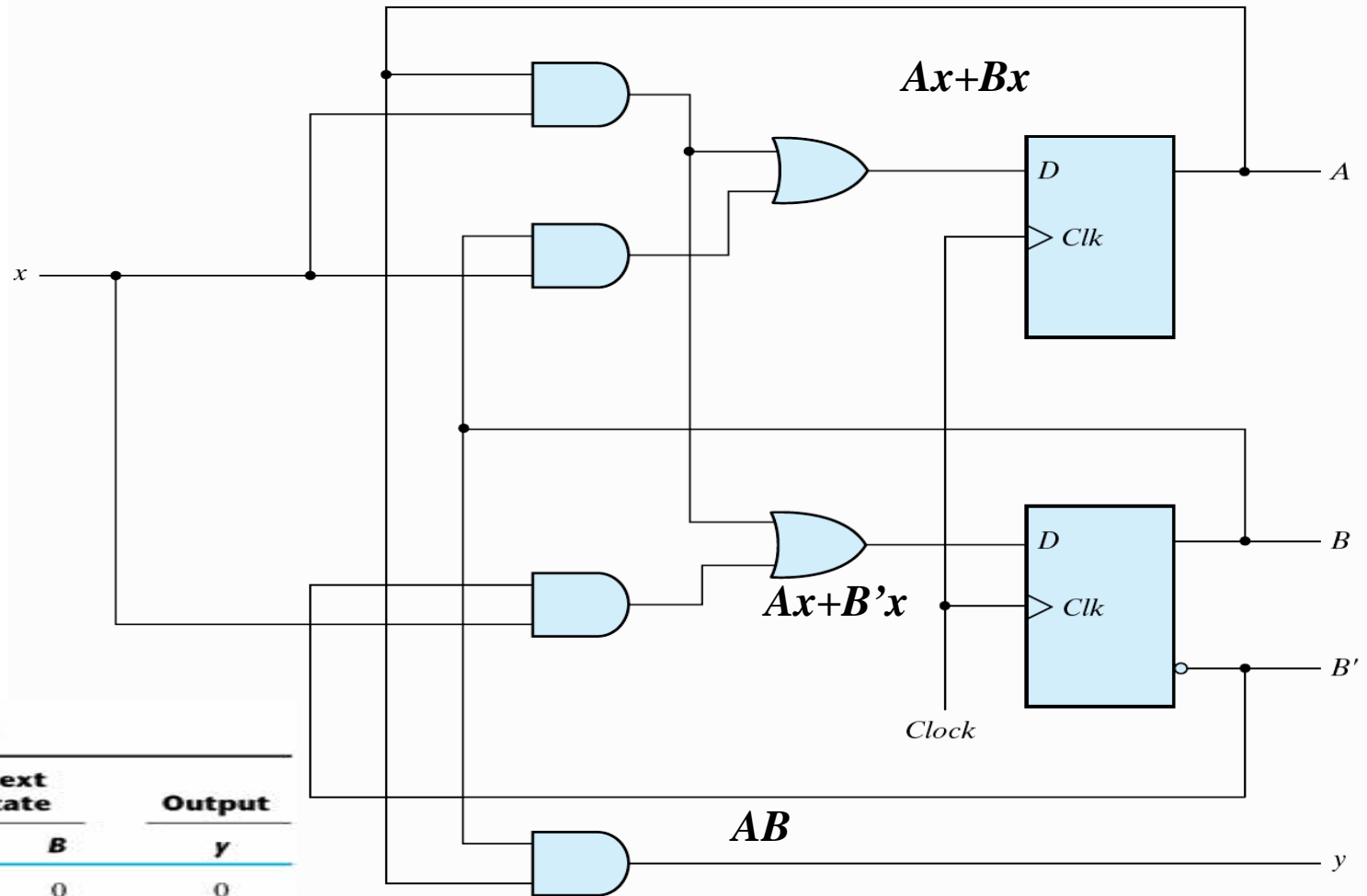


Table 5.11
State Table for Sequence Detector

Present State		Input <i>x</i>	Next State		Output <i>y</i>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

back

Synthesis using JK flip-flops (1/4)

- A state diagram \Rightarrow flip-flop input functions
 - straightforward for D flip-flops
 - we need excitation tables for JK and T flip-flops

J	K	D	Q(t+1)	Function
0	0	Q(t)	Q(t)	no change
0	1	0	0	reset FF to 0
1	0	1	1	set FF to 1
1	1	Q'(t)	Q'(t)	complement output

T	D	Q(t+1)	
0	Q	Q(t)	no change
1	Q'	Q'(t)	complement

Table 5.12
Flip-Flop Excitation Tables

Q(t)	Q(t = 1)	J	K	Q(t)	Q(t = 1)	T
0	0	0	X	0	0	0
0	1	1	X	0	1	1
1	0	X	1	1	0	1
1	1	X	0	1	1	0

(a) JK

(b) T

Synthesis using JK flip-flops (2/4)

- The same example
- The state table and JK flip-flop inputs

Table 5.13

State Table and JK Flip-Flop Inputs

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Synthesis using JK flip-flops (3/4)

		B			
		Bx	00	01	11
A	0	m_0	m_1	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 X	m_6 X
		x			
		$J_A = Bx'$			

		B			
		Bx	00	01	11
A	0	m_0 X	m_1 X	m_3 X	m_2 X
	1	m_4	m_5	m_7 1	m_6
		x			
		$K_A = Bx$			

		B			
		Bx	00	01	11
A	0	m_0	m_1 1	m_3 X	m_2 X
	1	m_4	m_5 1	m_7 X	m_6 X
		x			
		$J_B = x$			

		B			
		Bx	00	01	11
A	0	m_0 X	m_1 X	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 1	m_6
		x			
		$K_B = (A \oplus x)'$			

Synthesis using JK flip-flops (4/4)

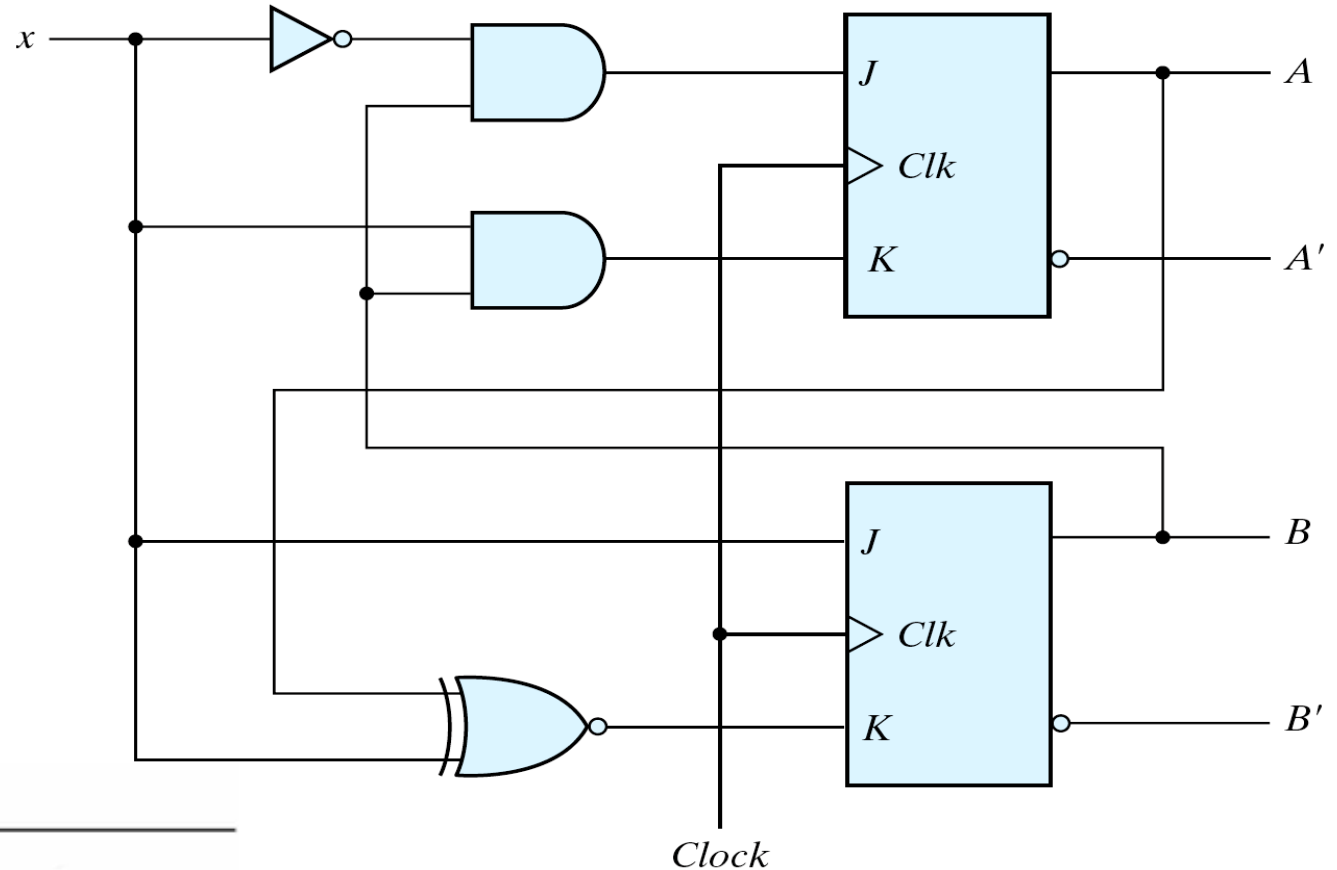



Table 5.13
State Table and JK Flip-Flop Inputs

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	X	0	X	
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Compare with D flip-flop

Synthesis using T flip-flops

 - A n-bit binary counter
 - the state diagram



- no inputs (except for the clock input)

The state table and the flip-flop inputs

Table 5.14

State Table for Three-Bit Counter

Present State			Next State			Flip-Flop Inputs		
A₂	A₁	A₀	A₂	A₁	A₀	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

No inputs (except for the clock input)

Logic Simplification using the K map

		A_1A_0		A_1	
		00	01	11	10
A_2	0	m_0	m_1	m_3 1	m_2
	1	m_4	m_5	m_7 1	m_6
		A_0			

$$T_{A_2} = A_1A_0$$


		A_1A_0		A_1	
		00	01	11	10
A_2	0	m_0	m_1 1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6
		A_0			

$$T_{A_1} = A_0$$

		A_1A_0		A_1	
		00	01	11	10
A_2	0	m_0 1	m_1 1	m_3 1	m_2 1
	1	m_4 1	m_5 1	m_7 1	m_6 1
		x			

$$T_{A_0} = 1$$


The Logic Diagram

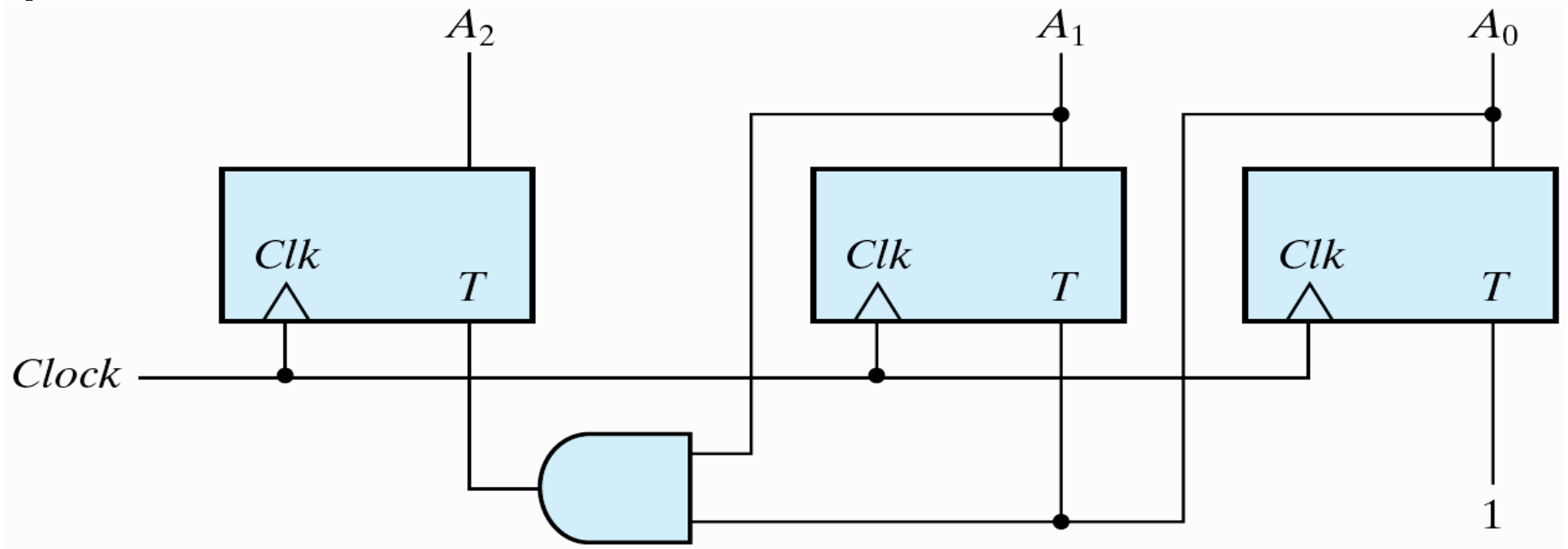

How to trace?


0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

Note:

 

Moore Machine (1/4)


Optimization flow

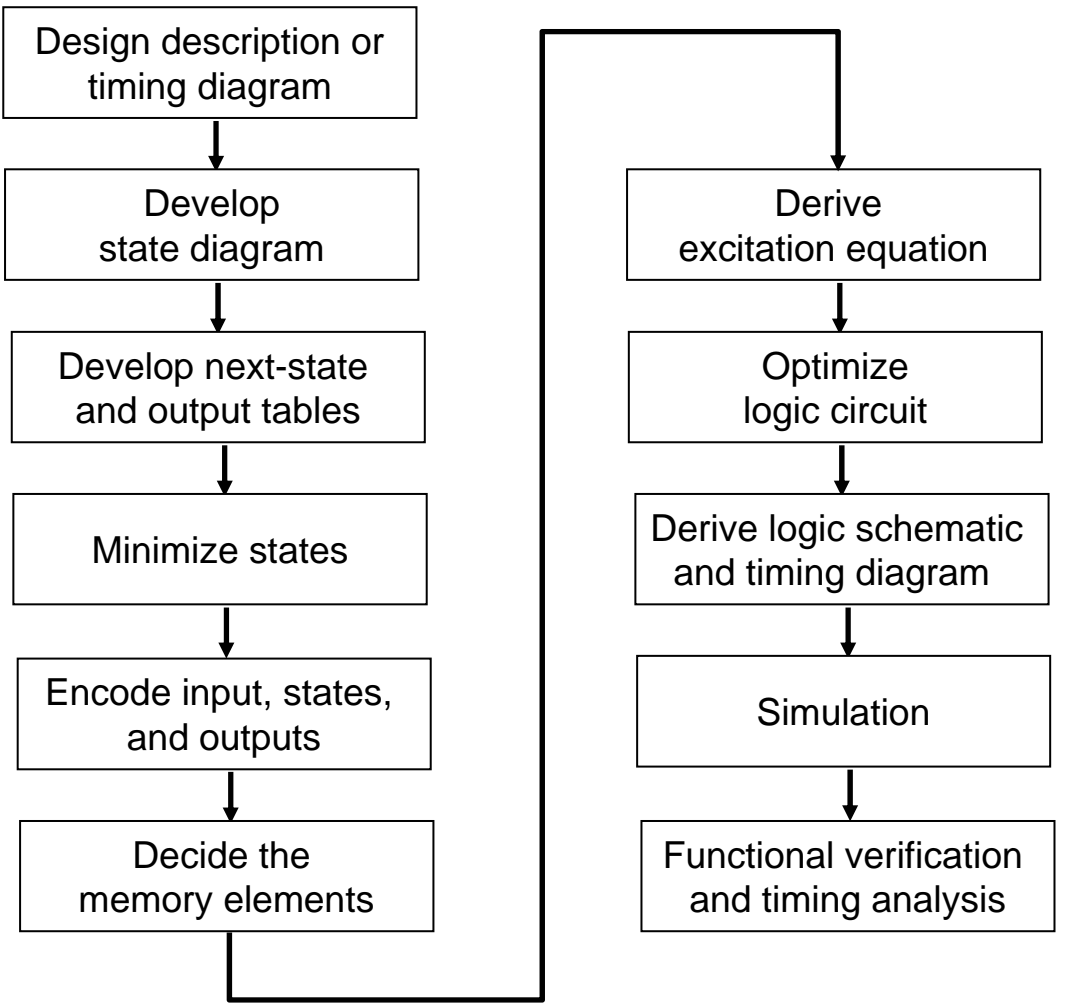

$S \rightarrow O$ S : state O : output

Next-state and output tables (I =input)

Present State	Next State		Output	
	$I=0$	$I=1$	$I=0$	$I=1$
S_0	S_0	S_2	0	0
S_1	S_0	S_2	1	1
S_2	S_2	S_3	1	1
S_3	S_3	S_1	0	0

 


Moore Machine (2/4)

original state table

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
S ₀	S ₀	S ₂	0	0
S ₁	S ₀	S ₂	1	1
S ₂	S ₂	S ₃	1	1
S ₃	S ₃	S ₁	0	0

 Assume that we use JK flip-flops for storage
 4 states \Rightarrow need 2 flip-flops (named M and N)



characteristic table

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

excitation table

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

I	Present State		Next State		M(JK)		N(JK)		Output
	M(t)	N(t)	M(t+1)	N(t+1)	MJ	MK	NJ	NK	
0	0	0	0	0	0	X	0	X	0
1	0	0	1	0	1	X	0	X	0
0	0	1	0	0	0	X	X	1	1
1	0	1	1	0	1	X	X	1	1
0	1	0	1	0	X	0	0	X	1
1	1	0	1	1	X	0	1	X	1
0	1	1	1	1	X	0	X	0	0
1	1	1	0	1	X	1	X	0	0

Moore Machine (3/4)

I \ MN		MN			
		00	01	11	10
I	0	0	0	X	X
	1	1	1	X	X

$$MJ=I$$

I \ MN		MN			
		00	01	11	10
I	0	X	X	0	0
	1	X	X	1	0

$$MK=NI$$

I \ MN		MN			
		00	01	11	10
I	0	0	X	0	X
	1	0	X	1	X

$$NJ=MI$$


I \ MN		MN			
		00	01	11	10
I	0	X	1	0	X
	1	X	1	0	X

$$NK=M'$$

I \ MN		MN			
		00	01	11	10
I	0	0	1	0	1
	1	0	1	0	1

$$\text{Output} = M'N + MN'$$



Next state logic

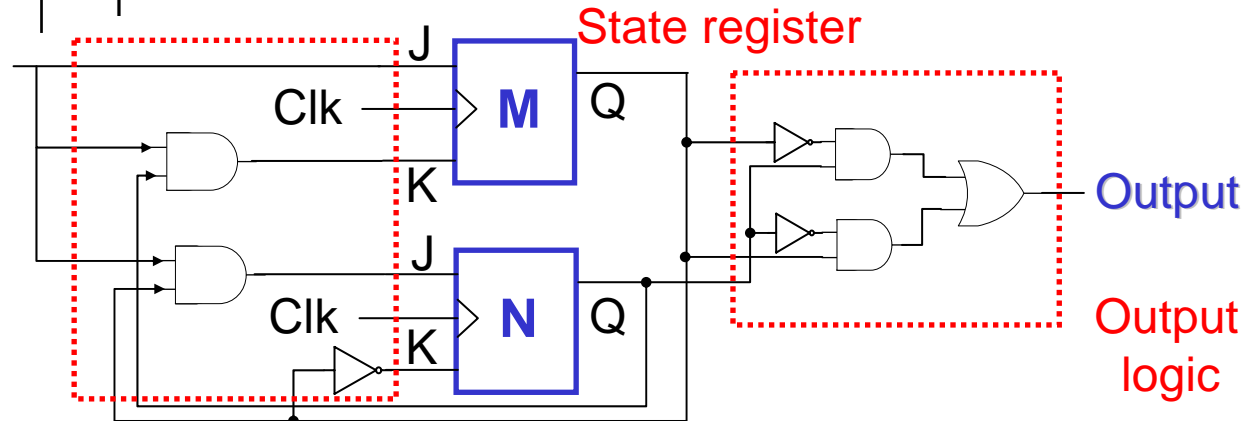

Moore Machine (4/4)

How about D Flip-Flop?

Which implementation is better?

  

I	Present State		Next State		Output
	A	B	A	B	
0	0	0	0	0	0
1	0	0	1	0	0
0	0	1	0	0	1
1	0	1	1	0	1
0	1	0	1	0	1
1	1	0	1	1	1
0	1	1	1	1	0
1	1	1	0	1	0

		AB			
		00	01	11	10
I	0	0	0	1	1
	1	1	1	0	1


So, $D_A =$

		AB			
		00	01	11	10
I	0	0	0	1	0
	1	0	0	1	1

So, $D_B =$

Output is the same as JK implementation.

Video Tape Player (1/2)

 

Video Tape Player (2/2)

